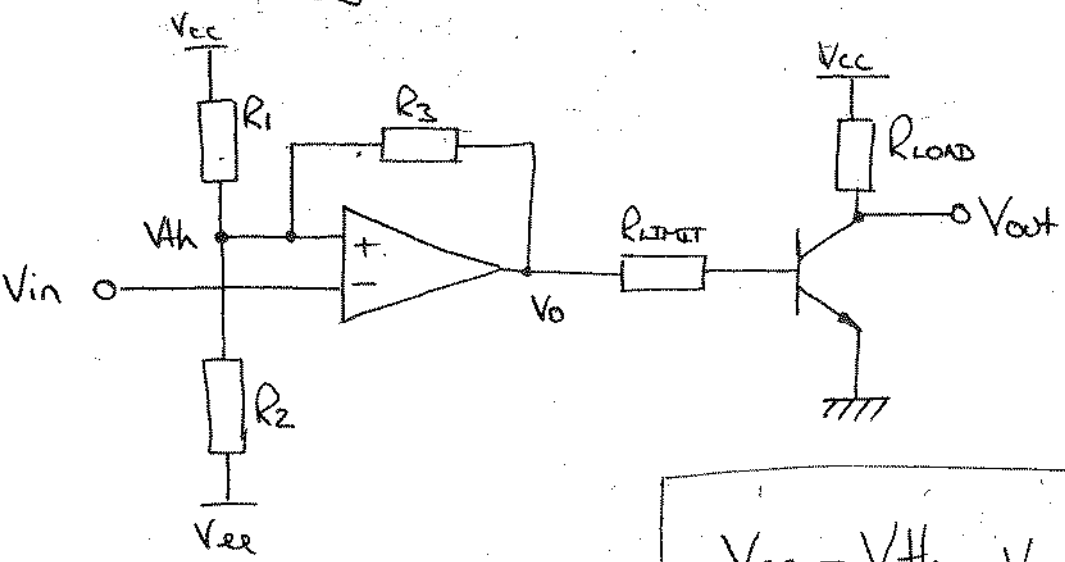


Schmitt Trigger

①

$$V = IR$$

$$\frac{V}{R} = I \quad \frac{V}{I} = R$$



Using Kirchoff's current law;

$$I_{R1} + I_{R3} - I_{R2} = 0$$

Using Ohm's law;

$$I_{R1} = \frac{V_{cc} - V_{th}}{R_1}$$

$$I_{R2} = \frac{V_{th} - V_{ee}}{R_2}$$

$$I_{R3} = \frac{V_o - V_{th}}{R_3}$$

$$\frac{V_{cc} - V_{th}}{R_1} + \frac{V_o - V_{th}}{R_3} - \frac{V_{th} - V_{ee}}{R_2} = 0$$

$$= \frac{R_2 \cdot R_3 (V_{cc} - V_{th})}{R_1 R_2 R_3} + \frac{R_1 R_2 (V_o - V_{th})}{R_1 R_2 R_3} - \frac{R_1 R_3 (V_{th} - V_{ee})}{R_1 R_2 R_3}$$

$$= \frac{R_2 R_3 V_{cc} - R_2 R_3 V_{th} + R_1 R_2 V_o - R_1 R_2 V_{th} - R_1 R_3 V_{th} + R_1 R_3 V_{ee}}{R_1 R_2 R_3}$$

$$= \frac{R_2 R_3 V_{cc} + R_1 R_2 V_o + R_1 R_3 V_{ee} - R_2 R_3 V_{th} - R_1 R_2 V_{th} - R_1 R_3 V_{th}}{R_1 R_2 R_3}$$

$$R_2 R_3 V_{cc} + R_1 R_2 V_o + R_1 R_3 V_{ee} = -(-R_2 R_3 V_{th} - R_1 R_2 V_{th} - R_1 R_3 V_{th})$$

$$R_2 R_3 V_{cc} + R_1 R_2 V_o + R_1 R_3 V_{ee} = V_{th} (R_1 R_2 + R_2 R_3 + R_1 R_3)$$

$$V_{th} = \frac{R_2 R_3 V_{cc} + R_1 R_2 V_o + R_1 R_3 V_{ee}}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$V_{th} = \frac{R_2 R_3 V_{cc} + R_1 R_2 V_o + R_1 R_3 V_{ee}}{R_1 (R_2 + R_3) + R_2 R_3}$$

© Andy Ash
2010

Now, we'd like to find the margin between thresholds;

$$V_{\text{margin}} = V_{\text{th}}(V_{\text{OH}}) - V_{\text{th}}(V_{\text{OL}})$$

$$V_{\text{th}} = \frac{R_2 R_3 V_{\text{CC}} + R_1 R_2 V_{\text{OH}} + R_1 R_3 V_{\text{EE}}}{R_1(R_2 + R_3) + R_2 R_3}$$

$$V_{\text{margin}} = \frac{A_1}{B} - \frac{A_2}{B} = \frac{A_1 - A_2}{B}$$

$$\begin{aligned} A_1 - A_2 &= R_2 R_3 V_{\text{CC}} + R_1 R_2 V_{\text{OH}} + R_1 R_3 V_{\text{EE}} - (R_2 R_3 V_{\text{CC}} + R_1 R_2 V_{\text{OL}} + R_1 R_3 V_{\text{EE}}) \\ &= R_1 R_2 V_{\text{OH}} - R_1 R_2 V_{\text{OL}} \\ &= R_1 R_2 (V_{\text{OH}} - V_{\text{OL}}) \end{aligned}$$

$$V_{\text{margin}} = \frac{R_1 R_2 (V_{\text{OH}} - V_{\text{OL}})}{R_1(R_2 + R_3) + R_2 R_3} \Leftarrow$$

Now we've found the margin between the thresholds, we'd like to find the centre of the space between the thresholds. This could be considered to be the "virtual threshold"

$$V_{\text{mid}} = \frac{V_{\text{margin}}}{2} + V_{\text{th}}(V_{\text{OL}}) = \frac{R_1 R_2 (V_{\text{OH}} - V_{\text{OL}})}{2R_1(R_2 + R_3) + 2R_2 R_3} + \frac{R_2 R_3 V_{\text{CC}} + R_1 R_2 V_{\text{OL}} + R_1 R_3 V_{\text{EE}}}{R_1(R_2 + R_3) + R_2 R_3}$$

all we need to do is simplify...

$$V_{mid} = \frac{(R_1(R_2+R_3)+R_2R_3)(R_1R_2(V_{OH}-V_{OL})) + (2R_1(R_2+R_3)+2R_2R_3)(R_2R_3V_{CC} + R_1R_2V_{OL} + R_1R_3V_{EE})}{(2R_1(R_2+R_3)+2R_2R_3)(R_1(R_2+R_3)+R_2R_3)}$$

$$V_{mid} = \frac{A+B}{C}$$

$$\begin{aligned} A &= R_1R_2(V_{OH}-V_{OL}) \cdot R_1(R_2+R_3) + R_1R_2(V_{OH}-V_{OL}) \cdot R_2R_3 \\ &= (R_1R_2V_{OH} - R_1R_2V_{OL})(R_1R_2 + R_1R_3) + (R_1R_2V_{OH} - R_1R_2V_{OL})R_2R_3 \\ &= R_1^2R_2^2V_{OH} + R_1^2R_2R_3V_{OH} - R_1^2R_2^2V_{OL} - R_1^2R_2R_3V_{OL} + R_1R_2^2R_3V_{OH} - R_1R_2^2R_3V_{OL} \end{aligned}$$

$$\begin{aligned} B &= (2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_2R_3V_{CC} + R_1R_2V_{OL} + R_1R_3V_{EE}) \\ &= 2R_1R_2^2R_3V_{CC} + 2R_1^2R_2^2V_{OL} + 2R_1^2R_2R_3V_{EE} \\ &\quad + 2R_1R_2R_3^2V_{CC} + 2R_1^2R_2R_3V_{OL} + 2R_1R_2^2R_3V_{EE} \\ &\quad + 2R_2^2R_3^2V_{CC} + 2R_1R_2^2R_3V_{OL} + 2R_1R_2R_3^2V_{EE} \end{aligned}$$

$$C = (2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_1R_2 + R_1R_3 + R_2R_3)$$

$$\begin{aligned} A &= R_1^2R_2^2(V_{OH}-V_{OL}) + R_1^2R_2R_3(V_{OH}-V_{OL}) + R_1R_2^2R_3(V_{OH}-V_{OL}) \\ &= V_{OH}(R_1^2R_2^2 + R_1^2R_2R_3 + R_1R_2^2R_3) - V_{OL}(R_1^2R_2^2 + R_1^2R_2R_3 + R_1R_2^2R_3) \end{aligned}$$

© Andy Ash
2010

$$B = 2V_{OL}(R_1^2R_2^2 + R_1^2R_2R_3 + R_1R_2^2R_3) + ((2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_2R_3V_{CC} + R_1R_3V_{EE}))$$

$$\begin{aligned} A+B &= V_{OH} + V_{OL}(R_1^2R_2^2 + R_1^2R_2R_3 + R_1R_2^2R_3) + ((2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_2R_3V_{CC} + R_1R_3V_{EE})) \\ &= (2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_2R_3V_{CC} + R_1R_2(V_{OH}+V_{OL}) + R_1R_3V_{EE}) \end{aligned}$$

$$\frac{A+B}{C} = \frac{(2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_2R_3V_{cc} + R_1R_2(V_{OH} + V_{OL}) + R_1R_3V_{ee})}{(2R_1R_2 + 2R_1R_3 + 2R_2R_3)(R_1R_2 + R_1R_3 + R_2R_3)}$$

$$= \frac{R_2R_3V_{cc} + R_1R_2(V_{OH} + V_{OL}) + R_1R_3V_{ee}}{R_1R_2 + R_1R_3 + R_2R_3}$$

$$V_{mid} = \frac{A+B}{C}$$

$$V_{mid} = \frac{R_2R_3V_{cc} + R_1R_2(V_{OH} + V_{OL}) + R_1R_3V_{ee}}{R_1(R_2 + R_3) + R_2R_3} \leftarrow$$

Notably V_{mid} & V_{th} are very similar functions. It was a lot of work to get V_{mid} , perhaps a better mathematician would have seen what now seems obvious!

© Andy Ash
2010.